



Date: 24/10/2018

Dept. No.

Max. : 100 Marks

Time: 09:00-12:00

**SECTION A**

**ANSWER ALL THE QUESTIONS**

**10 X 2 = 20**

1. How an SR flip flop is transformed into a D flip flop?
2. What are synchronous sequential circuits?
3. What is the need of a shift register?
4. Define an “n” bit register.
5. State the importance of computer instructions.
6. What are the three instruction code formats?
7. What is a Branch Unconditionally instruction?
8. State the function of the LDA instruction.
9. List down the various data transfer instructions.
10. What is a relative address mode?

**SECTION B**

**ANSWER ALL THE QUESTIONS**

**5 X 8 = 40**

11. a. Explain full adder with truth table and circuit diagram.

**(OR)**

- b. Simplify the following Boolean algebra

i.  $ABC + A'B'C + A'BC + A'B'C$

ii.  $XYZ + X'Y'Z + XY'Z'$

12. a. Explain about encoders in detail.

**(OR)**

- b. Write about multiplexers.

13. a. Discuss about various computer registers.

(OR)

b. Explain how the registers are connected to a common bus with a neat diagram.

14. a. Write about various register reference instructions.

(OR)

b. Explain about input/output configuration.

15. a. Discuss about the organization of status bit registers.

(OR)

b. Briefly explain about various data manipulation instructions.

### SECTION C

ANSWER ANY TWO QUESTIONS

2 X 20 = 40

16. a. Simplify the following

i.  $F(x,y,w, z) = \sum (0,2,4,6,12,14)$

ii.  $F(x,y,z) = \sum (0,1,4,5,6,7)$

b. Explain about binary counters with a neat diagram.

17. a. Explain about stored program organization.

b. Discuss on the fetch phase of the instruction cycle with a neat diagram.

18. a. Explain the way how interrupts are handled.

b. With a neat diagram explain the general register organization.

\*\*\*\*\*