



**LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034**

**M.C.A. DEGREE EXAMINATION – COMPUTER APPLICATIONS**

FIRST SEMESTER – NOVEMBER 2016

**CA 1807 - COMPUTER ORGANIZATION & ARCHITECTURE**

Date: 08-11-2016  
Time: 01:00-04:00

Dept. No.

Max. : 100 Marks

**PART-A**

**Answer ALL the questions**

**10\*2=20**

- 1) Write the truth table for XOR gate.
- 2) What are combinational circuits?
- 3) Mention the methods of simplifying Boolean expression.
- 4) Write a note on T flip flop.
- 5) What are the four types of micro-operations?
- 6) What are the basic types of computer instructions?
- 7) Why is an interface required between CPU and peripherals?
- 8) Bring out the difference between isolated and memory mapped I/O.
- 9) List out the replacement algorithms employed in cache memory.
- 10) Mention the basic components of a memory management unit.

**PART-B**

**Answer ALL the questions**

**5\*8=40**

- 11) a) Describe adders with neat diagram.  
(or)  
b) Explain decoder and encoder with diagram.
- 12) a) Give a detailed description on control unit  
(or)  
b) Explain 4 bit binary adder/subtractor with a neat diagram
- 13) a) Explain general register organization  
(or)  
b) Describe arithmetic and shift microoperations.
- 14) a) Explain DMA.  
(or)  
b) Explain Daisy Chaining.
- 15) a) Elucidate the mapping procedures in cache memory.  
(or)  
b) Explain crossbar switch and multistage switching network with diagrams.

**PART-C**

**Answer ALL Questions**

**2\*20=40**

- 16) Answer the following:  
a) Subtractors  
b) Any two flip flops  
(10+10)
- 17) Explain the following with required figures:  
a) Shift registers  
b) Addressing modes  
(5+15)
- 18) Give a detail explanation on  
a) Strobe and handshake  
b) RAM chip  
(15+5)

\*\*\*\*\*