



LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034

B.Sc. DEGREE EXAMINATION – PHYSICS

THIRD SEMESTER – APRIL 2014

PH 3106 - APPLIED ELECTRONICS

Date : 05/04/2014
Time : 09:00-12:00

Dept. No.

Max. : 100 Marks

PART A

Answer **ALL** the questions

(10 × 2 = 20)

1. What is Zener diode?
2. What is a depletion layer?
3. What is the output voltage of a summing amplifier when $V_1 = 2V$, $V_2 = 1V$, $R_1 = 10\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_f = 10\text{ k}\Omega$.
4. State any four properties of an ideal Op-amp
5. Simplify using K-map $F(A,B,C) = (0, 2, 4, 6, 7)$
6. What is a half adder?
7. What is a flip flop?
8. What are shift registers? Name the types
9. Write the difference between main memory and auxiliary memory.
10. State two differences between RAM and ROM

PART – B

Answer any **FOUR** questions

(4 × 7.5 = 30)

11. Write short notes on (i) intrinsic semiconductor (ii) extrinsic semiconductors (iii) PN junction diode
12. Explain the working of a summing amplifier with a neat diagram
13. a) Define Multiplexer.
b) Explain 4-1 multiplexer with logic circuit
14. With a neat diagram explain the working of a clocked RS flip-flop.
15. Name and explain the different types of registers in a computer.

PART – C

Answer any **FOUR** questions

(4 × 12.5 = 50)

16. Describe the operation of a NPN transistor in common emitter mode. Obtain the input and output characteristics for the same.
17. Explain with a neat diagram the working of a successive approximation A/D convertor
18. a) Simplify using K-map, $F(A,B,C,D) = _ (3,4,6,7,11,12,13,14,15)$ (8)
b) Simplify $Y = [AB (C + BD) + A B] C$ (4.5)
19. a) Explain the shift right shift register with a neat diagram (7.5)
b) How can we convert a JK Flip flop into (i) D flip flop (ii) T-Flip flop? (5)
20. a) Explain the various components in memory hierarchy using block diagrams (6.5)

b) Discuss in detail about Timing & control in a digital computer. (6)