

LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034**U.G. DEGREE EXAMINATION – ALLIED****FOURTH SEMESTER – APRIL 2023****UPH 4401 – APPLIED PHYSICS**

Date: 04-05-2023

Dept. No.

Max. : 100 Marks

Time: 09:00 AM - 12:00 NOON

SECTION A - K1 (CO1)**Answer ALL the Questions****(10 x 1 = 10)****1. Answer the following**

- a) Write down any two examples of semiconductors.
- b) Define LDR.
- c) Convert $(24)_{10}$ into a binary number.
- d) Draw the logic symbol of OR gate.
- e) What are the characteristics of LASER?

2. Fill in the blanks

- a) Intrinsic semiconductor is called _____.
- b) The principle of a solar cell is _____.
- c) In NAND gate, the output will be low when both the inputs are _____.
- d) In IC 741, pin 2 is _____.
- e) LASER works on the principle of _____.

SECTION A - K2 (CO1)**Answer ALL the Questions****(10 x 1 = 10)****3. True or False**

- a) Steel is an insulator.
- b) LED consume more electricity.
- c) The NOT gate is also known as an inverter.
- d) There are two outputs in an Op -Amp.
- e) He-Ne is a four level laser.

4. Match the following

- a) Compound semiconductor - invert the input
- b) Threshold frequency - $\bar{X} + \bar{Y}$
- c) Inverting Op-Amp - GaAs
- d) $\bar{X} \cdot \bar{Y}$ - optical pumping
- e) Ruby Laser - photoelectric effect

SECTION B - K3 (CO2)**Answer any TWO of the following****(2 x 10 = 20)**

5. a) What is biasing? (2)
b) Explain the forward and reverse biasing of a P-N junction diode and draw the characteristic curve. (8)
6. With neat diagrams explain the construction and working principle of photo diode and photo transistor.
7. Convert
a) $(1021)_{10}$ to binary (2)

	b) $(934)_{10}$ to octal	(2)
	c) $(111001)_2$ to Hex	(2)
	d) $(111011)_2$ to decimal	(2)
	e) $(1101011.1011)_2$ to decimal	(2)
8.	With neat circuit diagrams, explain the working of inverting and non-inverting amplifier operations of Op-Amp.	
SECTION C – K4 (CO3)		
	Answer any TWO of the following	(2 x 10 = 20)
9.	a) What is a semiconductor?	(2)
	b) Describe the classification of semiconductors.	(8)
10.	a) Simplify $Y = \overline{A} \overline{B} + \overline{A} B$	(3)
	b) $F(A,B,C) = ABC + \overline{A} \overline{B} C + \overline{A} B C + A B \overline{C} + \overline{A} \overline{B} A \overline{C}$	(7)
11.	a) Write down the characteristics of LASER.	(4)
	b) Discuss spontaneous and stimulated emission of radiation.	(6)
12.	Discuss the working of an Op-Amp as an integrator and differentiator.	
SECTION D – K5 (CO4)		
	Answer any ONE of the following	(1 x 20 = 20)
13.	Describe the construction and working principle of Nd:YAG laser with energy level diagram.	
14.	a) Explain the working of a Zener diode with neat diagram.	(12)
	b) Describe how a Zener diode can be used for voltage regulation.	(8)]
SECTION E – K6 (CO5)		
	Answer any ONE of the following	(1 x 20 = 20)
15.	a) With neat diagrams and truth tables, show that NAND is a universal gate.	(10)
	b) Convert the following hexadecimal numbers to decimal numbers i. $(E9)_H$ ii. $(FFFF)_H$ iii. $(604)_H$ iv. $(3FC.8)_H$	(10)
16.	Explain the operation of an Op-Amp as summing and difference amplifiers.	
