

LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034

U.G. DEGREE EXAMINATION – ALLIED
THIRD SEMESTER – NOVEMBER 2023
UPH 3403 – APPLIED ELECTRONICS

Date: 08-11-2023

Dept. No.

Max. : 100 Marks

Time: 09:00 AM - 12:00 NOON

SECTION A - K1 (CO1)**Answer ALL the Questions****(10 x 1 = 10)****1. Answer the following**

- a) What is a semiconductor?
 b) Draw the symbol of a diode.
 c) Write any one application of 555 timer.
 d) Define RAM.
 e) Draw the pin configuration of IC 741.

2. Fill in the blanks

- a) The most commonly used semiconductor is -----.
 b) LEDs operates at ----- bias.
 c) The depletion region in a semiconductor pn junction diode has -----.
 d) Op amp has ----- gain.
 e) The function of pin 3 in IC 555 timer is -----.

SECTION A - K2 (CO1)**Answer ALL the Questions**
10)**(10 x 1 =****3. True or False**

- a) The reverse breakdown voltage of LED is very low.
 b) Schmitt trigger is an application of IC 555 timer.
 c) CMRR stands for common mode reverse ratio.
 d) Data and instructions are stored in RAM.
 e) Zener breakdown occurs in thick region.

4. MCQ

- a) Op-Amp is a ----- type of amplifier.
 (a) Current (b) voltage (c) power (d) resistance
 b) The memory in which the stored data is lost, when power is switched off is -----
 (a) RAM (b) ROM (c) PROM (d) EPROM
 c) 555 timer consists of -----comparators.
 (a) Three (b) two (c) five (d) one
 d) How many resistors are used in inverting amplifier?
 (a) three (b) two (c) one (d) five
 e) A Semiconductor PN Junction device which converts light energy into _____ energy.
 (a)mechanical (b) electrical (c)heat (d) sound

SECTION B - K3 (CO2)

Answer any TWO of the following (2 x 10 = 20)

5. What is extrinsic semiconductor? Distinguish between n-type and p-type semiconductors. Draw relevant energy level diagram.
6. Explain with a neat diagram, the working of an inverting amplifier.
7. Write a note on magnetic memory.
8. With a neat diagram, explain the working of a Schmitt trigger using IC-555.

SECTION C – K4 (CO3)

Answer any TWO of the following (2 x 10 = 20)

9. Explain the I-V characteristics of Zener diode. Mention its uses.
10. With a neat diagram, explain the working of an Astable multivibrator using IC 555 timer.
11. What is meant by semiconductor memory? Explain its types.
12. Elucidate on the working of a non – inverting amplifier.

SECTION D – K5 (CO4)

Answer any ONE of the following (1 x 20 = 20)

13. Explain in detail, the principle, operation and applications of a Photo diode.
14. Explain how an op-amp can be used as, i) a summing and ii) difference amplifier.

SECTION E – K6 (CO5)

Answer any ONE of the following (1 x 20 = 20)

15. (a) Draw the internal block diagram and pin configuration of IC 555 timer and explain its working.
(b) Write down the characteristics of an ideal op amp. (12+8 marks)
16. What is a p-n junction? Explain the formation of the depletion region in a p-n junction. How does the width of this region change when the junction is (i) forward biased (ii) reverse biased?

#####