

4.	True or False
a)	Both OR and AND gates can have only two inputs
b)	The standard form of S-R flip flop is Set-Reset
c)	All the rules for Boolean algebra are exactly the same as for ordinary algebra
d)	$A + 0 = 0$
e)	Mod-N counter is a counter that goes through a repeated sequence of N counts

SECTION B - K3 (CO2)

	Answer any TWO of the following in 100 words	(2 x 10 = 20)
5.	$(29)_{10} = (X)_8 = (Y)_{16} = (Z)_2$, Find X,Y,Z	
6.	Apply the laws of boolean algebra Show that (i) $(\bar{A} + B)(\bar{B} + C)(\bar{C} + A) = (A + \bar{B})(B + \bar{C})(C + \bar{A})$ (ii) $AB + \bar{A}C + BC = AB + \bar{A}C$	(5 marks) (5 marks)
7.	Design a K-map and give the expression. (i) $Y = F(A,B,C,D) = \sum(0,2,4,6,7)$ (ii) $Y = F(A,B) = \sum(2,3)$	(5 marks) (5 marks)
8.	Draw and explain the working of a UP counter and give its truth table	

SECTION C – K4 (CO3)

	Answer any TWO of the following in 100 words	(2 x 10 = 20)
9.	Draw the logic gates AND, OR, NOT, NAND and NOR and explain it with appropriate truth tables	
10.	Evaluate using K map $Y = F(A, B, C, D) = \sum(0,1,3,5,7,9,11,12,13,14,15)$	
11.	Analyse the working of a D- Flip flop with the circuit diagram using NAND gate	
12.	Define (i) positive and negative logic (ii) SOP with an example (iii) Flip flop	(4 marks) (3 marks) (3 marks)

SECTION D – K5 (CO4)

	Answer any ONE of the following in 250 words	(1 x 20 = 20)
13.	(i) Explain the working of a shift left shift register with a neat diagram and truth table (ii) Draw the circuit diagram of Mod 4 and Mod 8 counters and explain its working	(10 marks) (10 marks)
14.	Convert (Each carries 4 marks) (i) $(10011.1011)_2$ into decimal. (ii) $(65.534)_{10}$ into hex. (iii) $(1F.2B4)_H$ to binary (iv) $(23.625)_8$ to decimal. (v) $(1011.11)_{10}$ to binary	

SECTION E – K6 (CO5)

	Answer any ONE of the following in 250 words	(1 x 20 = 20)
15.	(i) Describe the working of JK flip flop with a neat diagram and truth table. (ii) Explain the circuit of NAND latch with neat circuit and truth table.	(10 marks) (10 marks)
16.	With the suitable circuit diagrams, show that NAND and NOR gates are universal gates.	

#####